

Kennesaw State University (KSU)
College of Computing and Software Engineering (CCSE)
CS-3503 Computer Organization & Architecture

Lab-2&3: A 5-bit Digital Memory & Computer Design

Pre-lab (Required)

- Getting ready – NI Multisim

Multisim is industry standard SPICE simulation and circuit design software for analog, digital, and power electronics in education and research.

1. Please use the web link below to **install it on yours** Windows OS based computer (Mac OS and Linux distributions cannot install it).

<https://www.ni.com/en/support/downloads/software-products/download.multisim.html#452133>

Create a student account and download and install (needs Windows 10 64-bit or use a VM such as VMWare Horizon Client from KSU on Mac) from the link above. If the KSU does not provide a Multisim license (you can check that in your student profile of UITS Software OnTheHub WebStore or here: <https://kennesaw.onthehub.com/WebStore/ProductsByMajorVersionList.aspx>), then a trial version of 45 days is available for free from NI.

A student could use both the NI Multisim 14 and MS Visual Studio 2022 via:

2. the CCSE Tutoring Center at Room J-263 has **KSU computers** which have native installations, or
3. the CCSE Virtual Desktop on <https://cseview.kennesaw.edu/> to install **VMWare** Horizon Client, the instructions to use this are provided in a separate document on the D2L.

Helpful Online Resources (Optional)

- Getting started – Multisim related videos (all links work when this document is posted, but a video may have been removed later on and hence, some link may not be functional later on):

Multisim: Brief Introduction: <https://www.youtube.com/watch?v=B8EwjRDZa6k>

Multisim: Basic Logic Gates: <https://www.youtube.com/watch?v=rflzjtZrBec>

A Digital Circuit: <https://www.youtube.com/watch?v=jwvM5Zt9kkc>

XOR: <https://www.youtube.com/watch?v=dl8a1heSk1U>

NAND: <https://www.youtube.com/watch?v=lm0CdSSQiAQ>

Decoder: <https://www.youtube.com/watch?v=7rhQwNeEc4o>

MUX: <https://www.youtube.com/watch?v=JyB7R8ToW3Y>

Half-Adder: <https://www.youtube.com/watch?v=ijlDYFePnrw>

Full Adder: <https://www.youtube.com/watch?v=bgRvQas0ZHI&t=2s>

DFF: https://www.youtube.com/watch?v=_hX2_q8qyTs

Shift Register: <https://www.youtube.com/watch?v=BdliATa-uEQ>

Counter: <https://www.youtube.com/watch?v=XYVzg-BGD7M>

Overall Specifications

In these two labs, you will be individually creating and simulating, utilizing an industry standard digital circuit simulator software Multisim® of the National Instruments (NI®), a stored-program computer (more specifically, von Neumann architecture where program instructions and data share the single memory space, hence the program can be modified during its execution; it would also use the same data and address buses) with the following specifications:

1. This computer will be based on the Load-Store hybridized with the Accumulator (AC register) machine architecture.
 - a. The first operand (of any operation involving two input operands) will be copied into the AC by a memory read of appropriate location when a Load (see below) instruction is executed.
 - b. An arithmetic or logical (see below) instruction's execution will involve the second operand (of any operation involving two input operands) to be copied into the Memory Buffer Register (MBR) first by a memory read of appropriate location.
 - c. The result of an arithmetic or logical operation will be computed through ALU, and temporarily stored in the AC updated right afterwards.
 - d. The result of an operation will be copied from the AC to a memory location by memory write operation when a Store (see below) instruction is executed.
2. It will have 5-bit machine architecture, i.e. each CPU instruction/data register and every memory location will be of 5-bit machine word size.
3. There will be 2-bit opcode in each instruction, hence there will be four instructions possible that could be executed by this computer. These instructions mnemonics along with their binary opcode will be as follows: Load=00, Store=01, Add=10, and AND=11.
4. It is going to have a single operand-based Instruction Set Architecture (ISA) that will use Direct Memory Addressing mode only. Hence, the 3-bit operand (could be a label just like MARIE assembly programming language) field in an instruction will be the memory address of the operand directly involved.
5. Please store the following two programs (one at a time and demonstrate it before switching to the other one) at the given binary addresses in the memory of your implementation:


		<u>Program-1</u>	<u>Program-2</u>
000		Load A	Load A
001		Add B	AND B
010		Store C	Store D
011			
100	A	00111	00111
101	B	00110	00110
110	C	00000	00000
111	D	00000	00000

Lab-2: A 5-bit Digital Memory Design


What and how to do?

In this lab, you are individually creating in NI Multisim the following:

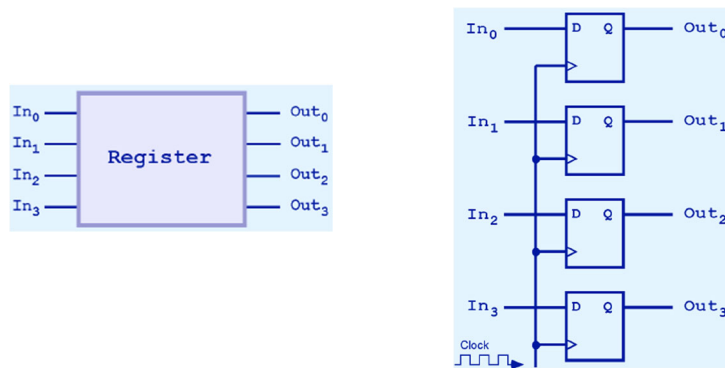- I. A memory with 3-bit addressable (hence, eight locations in total) and 5-bit word size at each location. Each bit of a word is going to be a D-flip-flop. For example, a 4-bit memory location (a register, shown below as well, is nothing but a local memory in the CPU for temporary storage just before an operations execution and hence, is exactly like a memory location) implementation is shown next.



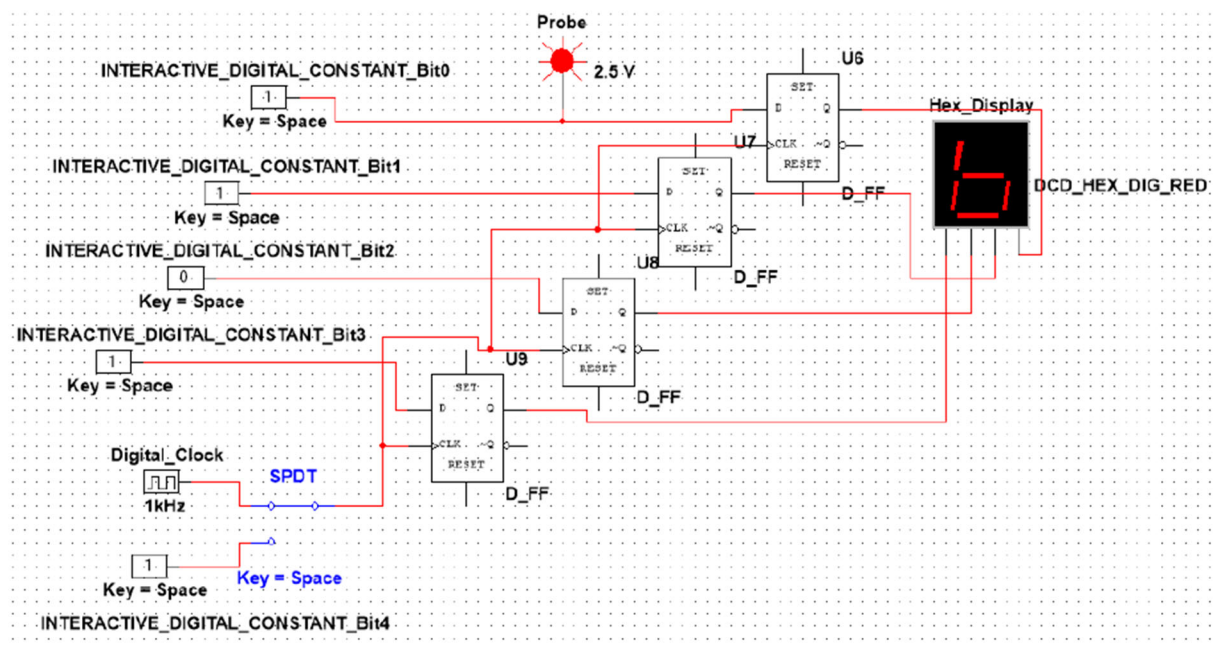
For reference, a Multisim implementation for a 4-bit word storage for a register or a memory location along with input means and contents' display is shown next.




Please note the manually controllable switch (SPDT) to select between manually and automatically D-flip flops' update (recall that flip flop memory update happens on the

low to high or rising edge signal) provision via Constant and Clock respectively. A bit data input for storage can be fed to a flip-flop using Constant. A nibble (4-bits combined) stored can be shown using a DCD_Hex_Dig_Red display.

 
- II. A 3-bit (hence, 3-to-8) **Decoder** (shown below to the left) with $n=3$ lines on the input side (which will be connected later to the Memory Address Register MAR in the CPU), and $2^n=8$ lines on the output of it. Each output line will be a switched-on Minterm at a time to address and **write** a particular memory location once the write-enabled clock signal arrives. An example 2-to-4 decoder circuit implementation is shown below to the right for reference.




This is a 2-to-4 decoder :

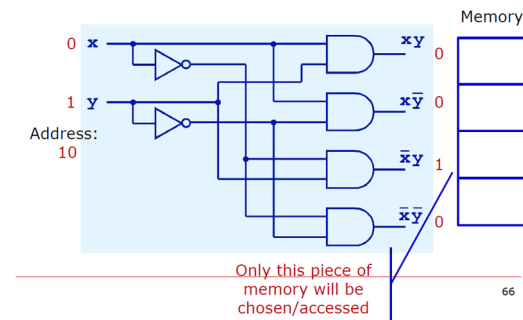

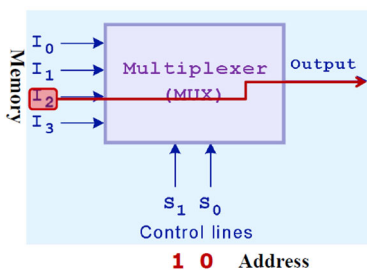
- III. A 3-bit (hence, 8-to-1) **Multiplexer** (shown below to the left is a 2-bit 4-to-1 Multiplexer) with $n=3$ lines on the address/control side (which will be connected later to the Memory Address Register MAR in the CPU), and $2^n=8$ lines on the input of it which will be connected to each memory location one-to-one from first to last memory location. The only output line is a bus (the parallel lines connecting a full word at a memory address to a full data register in the CPU LSb-to-LSb, MSb-to-MSb, and all other bits in the same fashion) to **read** a memory location's contents. An example 4-to-1 multiplexer circuit implementation is shown below to the right for reference.



□ This is a 4-to-1 multiplexer.

 


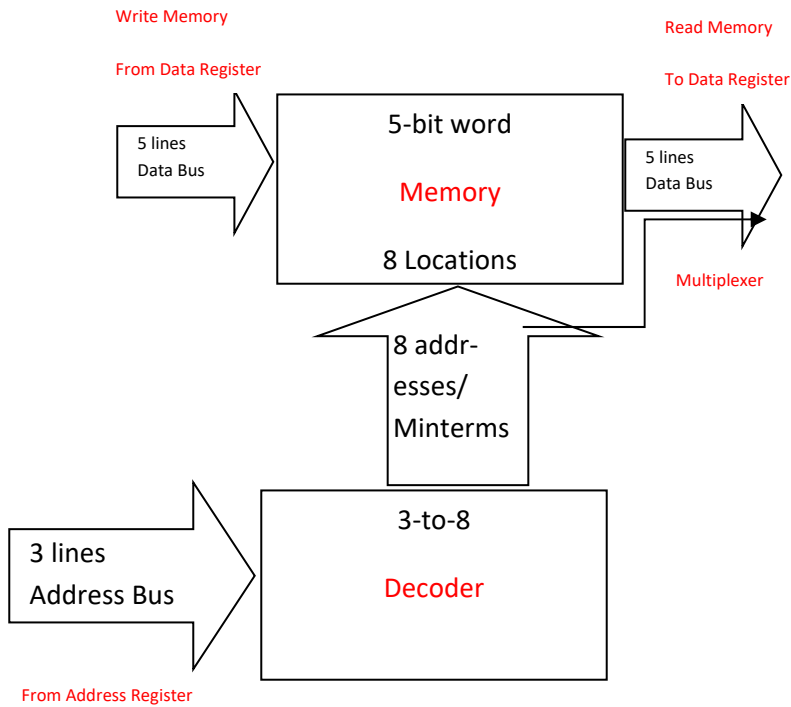At this time, you should have a completely connected, functional, addressable Memory unit (see below a reference block diagram showing this) which would be capable of letting you read or write a 5-bit data if 3-bit address is given.



An example 2-bit address and 3-bit Word based Memory unit circuit implementation is shown below for reference.

3.6 4X3 Memory

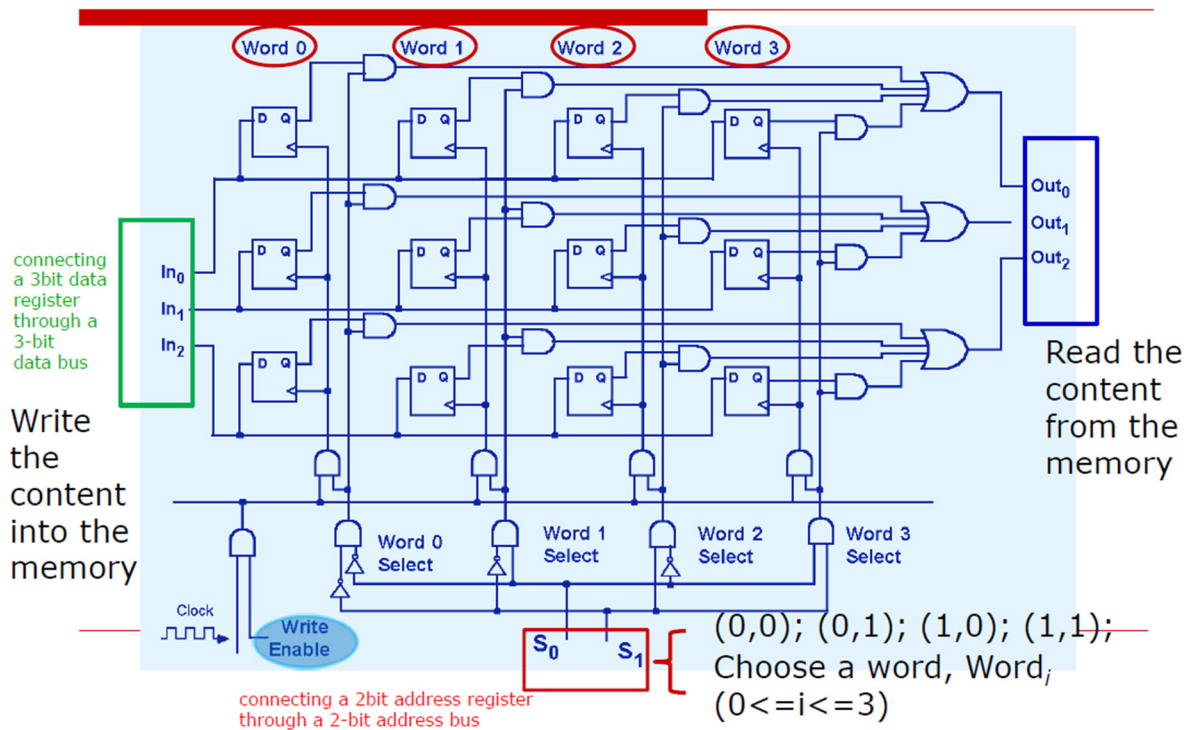

WHAT TO SUBMIT?

You will submit (by the deadline on the D2L) **one Multisim file** and a **MS Word/PDF file** that will document **four images** in the order below.

- i. A full screenshot of Multisim canvas on which decoder, memory and multiplexer are present as per design specifications above.
- ii. A focused screenshot of Multisim canvas on which the decoder is present as per the design specifications above.
- iii. A focused screenshot of Multisim canvas on which the multiplexer is present as per the design specifications above.
- iv. A focused screenshot of Multisim canvas on which the memory unit is present as per the design specifications above and all memory locations are setup such that they contain Program-1.